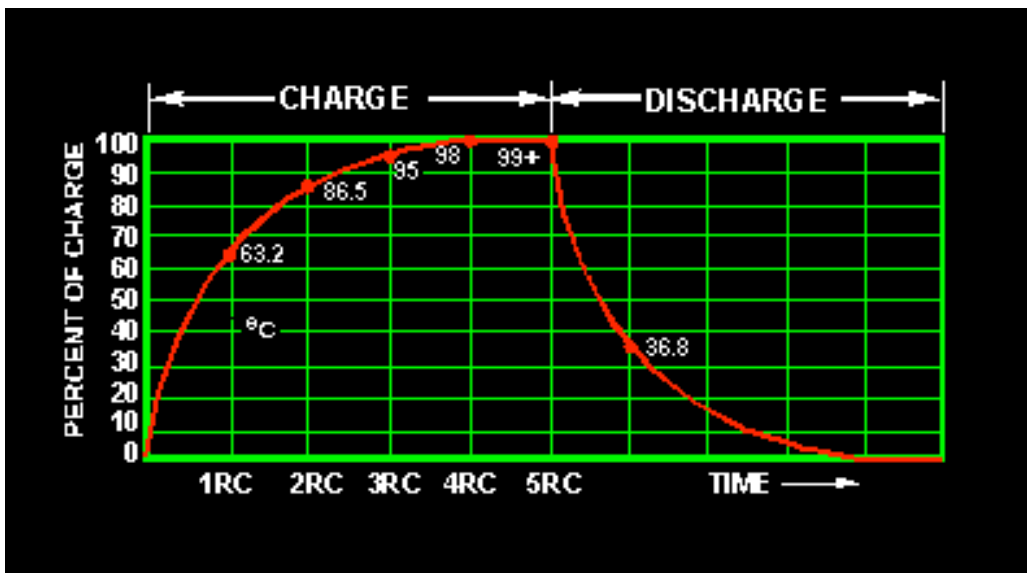


AC Circuits PHYS 401 Homework 3

NAME: _____ Due: November 1, 2010

Excellent reference: <http://tpub.com/neets/book2/3.htm>

1. An “RC” circuit has a resistor, a capacitor, and a power source in series. It exponentially charges its capacitor when a voltage is applied suddenly to the circuit. The current starts out large (as if there were no capacitor) but then trails off exponentially. When the charge on the capacitor equals the voltage on the source, the current stops. Similarly, when you then turn off the external voltage source, the current again flows, exponentially decreasing in current and in remaining charge on the capacitor. The time constant for the charging or discharging is called the “RC” time constant, and is equal to RC, the resistance in Ohms times the Capacitance in Farads.



As this graph shows, the charging (or discharging) is essentially complete after 5 RC time periods.

A circuit such as this is called a “HIGH-PASS” circuit, allowing frequencies above $1/RC$ to pass but stopping frequencies below $1/RC$.

Note that for a circuit with a capacitor, the voltage LAGS the current – the current goes up first, then the voltage. We remember this by “ICE”: I is before E in a CAPACITOR.

For a circuit with a resistor of $10\text{ K}\Omega$ and a capacitor of 5 microFarads , what is the time

constant? _____ s What if the capacitor is 5 milliFarads ? _____ s.

Which one will store the most charge? _____

What cutoff frequency is that for each? _____ Hz and _____ Hz.

2. What is the total capacitance of a 5 mF and a 10 mF capacitor in parallel?

_____ in series? _____

Good reference: <http://tpub.com/neets/book2/4.htm>

3. An inductor is similar, except that the Voltage leads the Current. "ELI": E is before I in an L-circuit.

The time constant for an inductive circuit (with a voltage, a resistor, and an inductor) is L/R , where R is the resistance in Ohms and L is the inductance in Henrys.

Capacitors and Inductors are said to have "Reactance" – like resistance but out of phase.

The reactance of a Capacitor is $X_C = 1/2\pi fC$ (often written as negative)

The reactance of an Inductor is $X_L = 2\pi fL$ (C is measured in Farads, L in Henrys, f in Hz)

What is the total inductance of a 2 Henry and 5 Henry inductor in series? _____

In Parallel? _____

4. An "LC" circuit has a resistor, inductor, and capacitor in series. This is a "tuned" circuit, that has minimum reactance at a specific frequency. First the capacitor builds up energy in charge and then the inductor builds up energy in magnetic field.

The total Reactance is $|X_C - X_L|$
 The net is always shown as positive, and if the inductive is larger, the net is inductive; if the capacitive is larger, the net is capacitive. So to make that minimum, you want

$$X_C = X_L \quad \text{so, } (2\pi f)^2 = 1/LC$$

$$\text{So } f = 1 / (2\pi (\text{sqrt } LC))$$

If you drive the circuit exactly at it resonance frequency, it will "ring" with minimum loss.

Now, for our cheapie AM radio, we want to tune for 740KHz. If the capacitor is 1 microFarad, what would the effective inductance of the coil be? (note: It's actually 120 pF)

(show your work!)

